

# Lecture IV: LTI models of physical systems

Maxim Raginsky

BME 171: Signals and Systems  
Duke University

September 5, 2008

# This lecture


Plan for the lecture:

- 1 Interconnections of linear systems
- 2 Differential equation models of LTI systems
- 3 Review of linear circuit theory
  - resistors, inductors, capacitors
  - Kirchhoff's laws
- 4 Examples of RLC circuits
- 5 Leaky integrate-and-fire (LIF) neuron

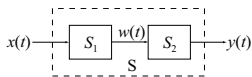
# Interconnections of linear systems

Linearity is preserved when systems are interconnected.


- **cascade:**  $S\{x(t)\} = S_2\{S_1\{x(t)\}\}$




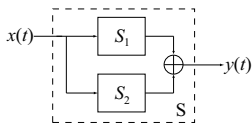- **sum:**  $S\{x(t)\} = S_1\{x(t)\} + S_2\{x(t)\}$



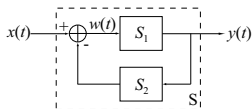- **feedback**  $S\{x(t)\} = S_1\{x(t) - S_2\{y(t)\}\}$



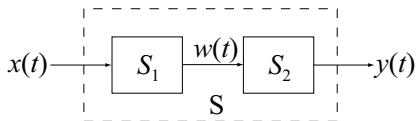


Let  $w(t)$  be the output of  $S_1$ . Then we first use linearity of  $S_1$ :

$$w(t) = S_1 \{ a_1 x_1(t) + a_2 x_2(t) \} = a_1 S_1 \{ x_1(t) \} + a_2 S_1 \{ x_2(t) \}$$

Now use linearity of  $S_2$ :


$$\begin{aligned} S \{ a_1 x_1(t) + a_2 x_2(t) \} &= S_2 \{ w(t) \} = S_2 \{ a_1 S_1 \{ x_1(t) \} + a_2 S_1 \{ x_2(t) \} \} \\ &= a_1 S_2 \{ S_1 \{ x_1(t) \} \} + a_2 S_2 \{ S_1 \{ x_2(t) \} \} \\ &= a_1 S \{ x_1(t) \} + a_2 S \{ x_2(t) \} \end{aligned}$$

This proves that  $S$  is linear.

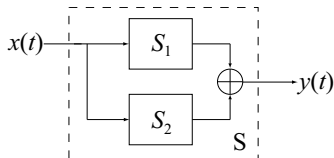

$$\begin{aligned}
 & S\{a_1x_1(t) + a_2x_2(t)\} \\
 &= S_1\{a_1x_1(t) + a_2x_2(t)\} + S_2\{a_1x_1(t) + a_2x_2(t)\} \\
 &= \underbrace{a_1S_1\{x_1(t)\} + a_2S_1\{x_2(t)\}}_{\text{use linearity of } S_1} + \underbrace{a_1S_2\{x_1(t)\} + a_2S_2\{x_2(t)\}}_{\text{use linearity of } S_2} \\
 &= a_1 \underbrace{(S_1\{x_1(t)\} + S_2\{x_1(t)\})}_{=S\{x_1(t)\}} + a_2 \underbrace{(S_1\{x_2(t)\} + S_2\{x_2(t)\})}_{=S\{x_2(t)\}} \\
 &= a_1S\{x_1(t)\} + a_2S\{x_2(t)\}
 \end{aligned}$$

This proves that  $S$  is linear.

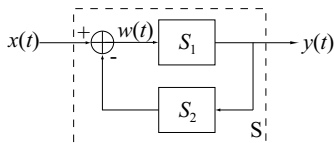

Let  $w(t) = x(t) - S_2\{y(t)\}$ . Now,  $y(t) = S_1\{w(t)\}$ , so

$$w(t) = x(t) - S_2\{S_1\{w(t)\}\} = x(t) - S\{w(t)\},$$

where  $S$  is the cascade of  $S_1$  and  $S_2$ , which is linear if both  $S_1$  and  $S_2$  are. The system  $S_3$  with input  $x(t)$  and output  $w(t)$ , defined by

$$w(t) = x(t) - S\{w(t)\},$$

is linear. Thus,

$$y(t) = S_1\{w(t)\} = S_1\{S_3\{x(t)\}\}$$

is a cascade of  $S_3$  and  $S_1$ , and so is linear.

# LTI systems via differential equations

A lot of continuous-time LTI systems are described by linear differential equations with constant coefficients:

$$\sum_{m=0}^M a_m \frac{d^m y(t)}{dt^m} = \sum_{n=0}^N b_n \frac{d^n x(t)}{dt^n}$$

where the coefficients  $\{a_m\}_{m=1}^M$  and  $\{b_n\}_{n=1}^N$  are independent of  $t$ .


Examples:

- linear electric circuits (RLC)
- mechanical systems (mass-spring-damper)

We will focus on electrical circuits.

# Review: linear circuit elements


**Resistor:**

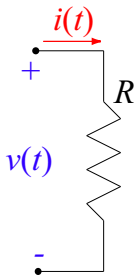

$$v(t) = Ri(t)$$

$$i(t) = \frac{v(t)}{R}$$


**Inductor:**

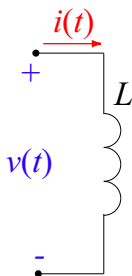

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

**Capacitor:**

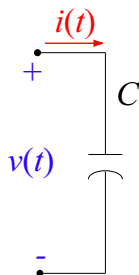


$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$



# Review: Kirchhoff's laws


**Kirchhoff's voltage law (KVL):**

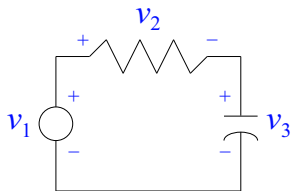

The sum of voltages in a loop is equal to zero:

$$-v_1 + v_2 + v_3 = 0$$


**Kirchhoff's current law (KCL):**

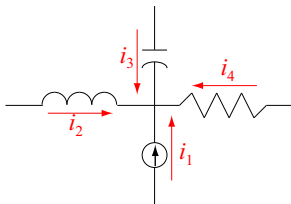

The sum of currents entering a node is equal to zero:

$$i_1 + i_2 + i_3 + i_4 = 0$$

## Example: Series RLC circuit

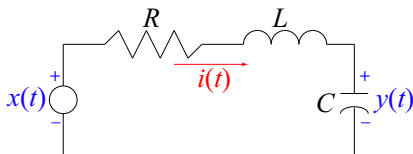

Input: voltage source  $x(t)$

Output: voltage across the capacitor  $y(t)$

Apply KVL:

$$-x(t) + Ri(t) + L\frac{di(t)}{dt} + y(t) = 0$$


Substitute  $i(t) = C\frac{dy(t)}{dt}$ :

$$-x(t) + RC\frac{dy(t)}{dt} + LC\frac{d^2y(t)}{dt^2} + y(t) = 0$$

Rearrange to get

$$LC\frac{d^2y(t)}{dt^2} + RC\frac{dy(t)}{dt} + y(t) = x(t)$$

## Example: Parallel RC circuit

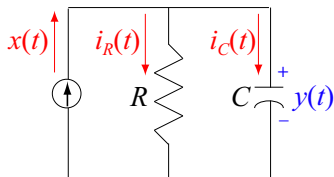

Input: current source  $x(t)$

Output: voltage across the capacitor  $y(t)$

Apply KCL:

$$x(t) = i_R(t) + i_C(t)$$

Substitute  $i_R(t) = \frac{y(t)}{R}$  and  $i_C(t) = C \frac{dy(t)}{dt}$ :



$$x(t) = \frac{y(t)}{R} + C \frac{dy(t)}{dt}$$

Rearrange to get

$$C \frac{dy(t)}{dt} + \frac{1}{R} y(t) = x(t)$$
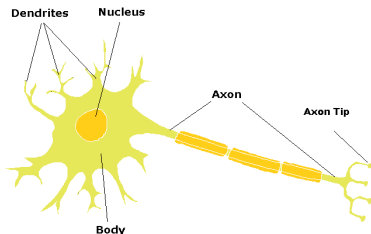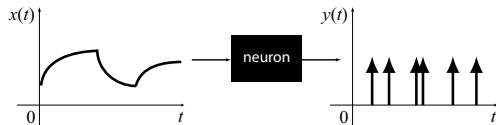
# Example: biological neurons

Biological neurons are highly nonlinear systems that convert incoming electrical signals (encoding external stimuli) into spike trains:



Inputs to the neuron are electrical signals traveling along the **dendrites** to the body (or **soma**) of the neuron. The neuron accumulates a potential (voltage) across its cell membrane and then **fires**, i.e., emits an electric pulse that travels down the **axon**.


# Leaky integrate-and-fire (LIF) neuron

The **leaky integrate-and-fire (LIF)** neuron is a simple model that describes the salient features of biological neurons. The LIF neuron has two distinct operating regimes:

- **subthreshold** — when the membrane potential of the neuron is below a certain threshold value  $V_{th}$ , the neuron acts like a parallel RC circuit. The capacitance is due to charge buildup on both sides of the bilipid layer that forms the cell membrane; the resistance is due to the presence of protein channels in the membrane that can carry  $K^+$ ,  $Na^+$  and  $Cl^-$  ions in and out of the cell (leakage current)
- **superthreshold** — when the membrane potential crosses  $V_{th}$ , the neuron “fires” (emits a unit impulse), and then short-circuits for  $\tau_{ref}$  seconds (the time known as the **refractory period**). After the refractory period elapses, the neuron returns to the subthreshold regime.
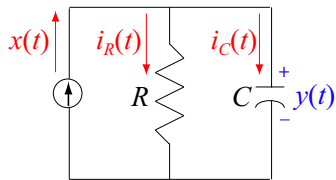
# Circuit model of the subthreshold regime

Let us look at the subthreshold regime of the LIF neuron with a unit step input  $x(t) = u(t)$



$$C \frac{dy(t)}{dt} + \frac{1}{R} y(t) = u(t)$$

$$y(t) = R \left[ 1 - e^{-t/RC} \right] u(t)$$

The overall output of the LIF neuron due to the unit step input looks like this:

